

 


Resistor-Transistor Logic (RTL)

 

RTL Inverter VTC

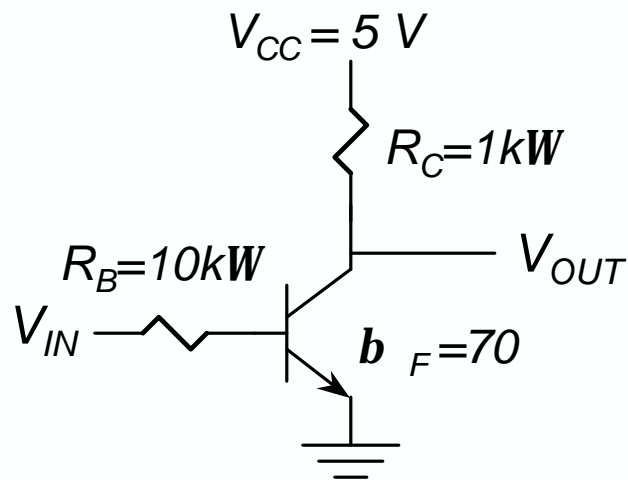


$$V_{OH} =$$

$$V_{IH} =$$

$$V_{OL} =$$

$$V_{IL} =$$

RTL Power Dissipation

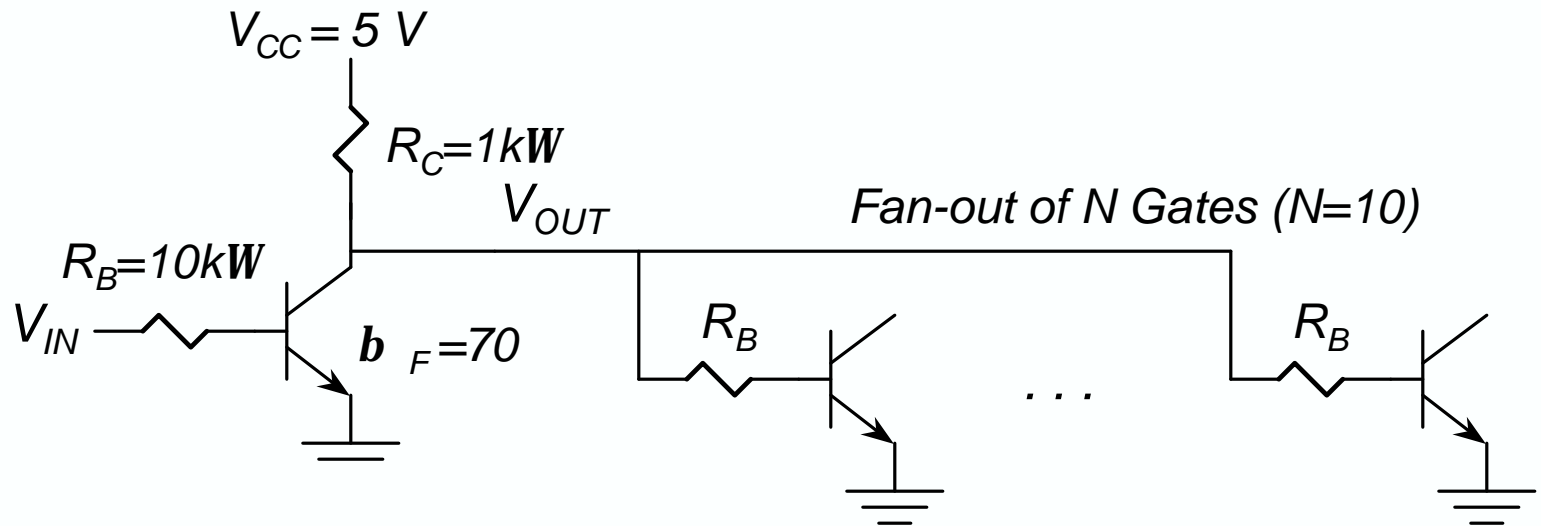


$$P_L =$$

$$P =$$

$$P_H =$$

RTL DC Fan-out

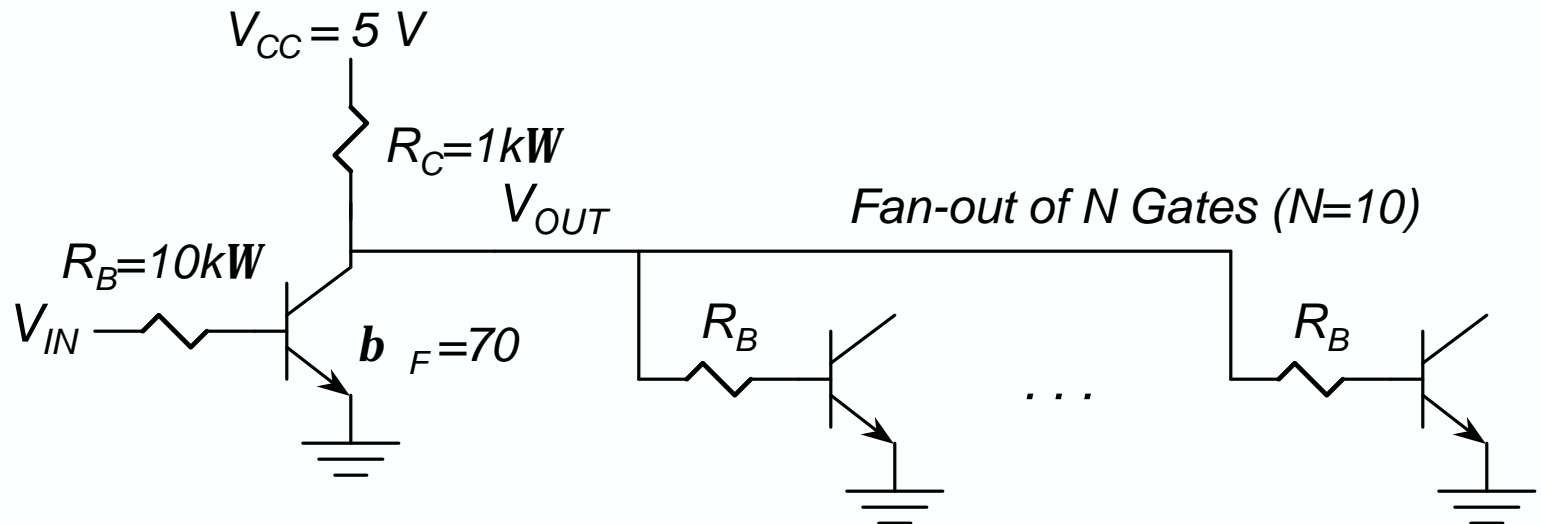

With a logic "1" output, the load gates draw current and reduce V_{OH} .

$$V_{OH} =$$

RTL DC Fan-out (continued)


The high noise margin goes to zero when $V_{OH} = V_{IH}$. This limitation determines the maximum fan-out N_{MAX} :

$$V_{OH} =$$

$$N_{MAX} \leq$$

In the present example, $N_{MAX} = 51$.

RTL Propagation Delays: t_{PHL}

 

The high-to-low propagation delay comprises the delay time and the fall time. Below, capacitive loading at V_{OUT} has been neglected.

Delay time
(cutoff operation):
$$t_d = \frac{V_{BEA}(C_{BE} + C_{BC})}{I_B(ave)}$$

Fall time
(active operation):
$$t_f = \frac{\Delta Q_F + \Delta V_{BC} C_{BC}}{I_B(ave)} = \frac{I_C(EOS)t_F + \Delta V_{BC} C_{BC}}{I_B(ave)}$$

RTL: t_{PHL} (cont.)

The junction capacitances are voltage-dependent, and SPICE takes this into account. For purposes of hand calculation, we use effective values: Thus if the voltage varies from V_1 to V_2 , then


$$C_J = \left(\frac{-C_{jo} f_o}{\Delta V (1-m)} \right) \left[\left(1 - \frac{V_2}{f_o} \right)^{1-m} - \left(1 - \frac{V_1}{f_o} \right)^{1-m} \right]$$

In calculating the delay time, V_{BE} varies from 0 to 0.7V. If $C_{JE0}=0.3\text{pF}$, $f_E=0.8\text{V}$, and $m_E=1/2$, then

$$C_{BE} =$$

Similarly, V_{BC} varies from -5V to -4.3V. If $C_{JC0}=0.15\text{pF}$, $f_C=0.8\text{V}$, and $m_C=1/3$, then $C_{BC} = 0.08\text{pF}$.


RTL Propagation Delays: t_{PHL}

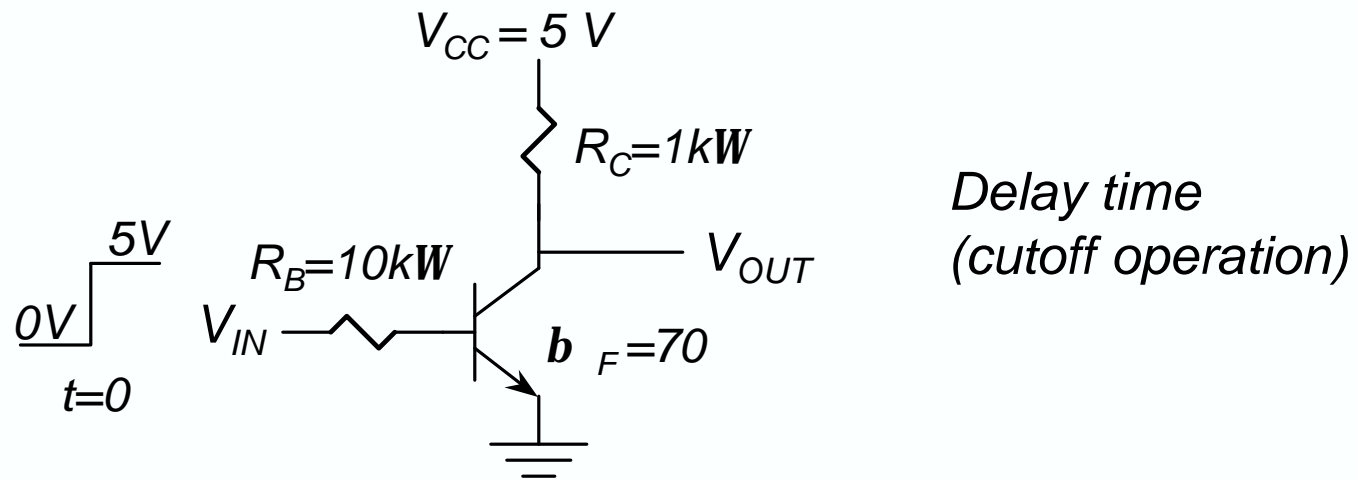

$$I_B(ave) =$$

$$t_d =$$

RTL Propagation Delays: t_{PHL}

 


V_{BC} varies from $-4.3V$ to $+0.5V$, so that $C_{BC} = 0.11pF$. With $t_F = 0.2 ns$,

$$t_f =$$

The high-to-low propagation delay is $t_{PHL} =$

RTL Propagation Delays: t_{PLH}

 

The low-to-high propagation delay comprises the saturation delay and the rise time. Again, capacitive loading at V_{OUT} has been neglected.


Saturation delay (sat. operation):
$$t_s = t_s \ln \left(\frac{I_{BF} - I_{BR}}{I_C(EOS) / b_F - I_{BR}} \right)$$

t_s is the “saturation time constant.”

Rise time (active operation):
$$t_r = \frac{I_C(EOS)t_F + |\Delta V_{BC}C_{BC}|}{|I_B(ave)|}$$

Under no-load, the numerator is the same as for t_f .

RTL Propagation Delays: t_{PLH}

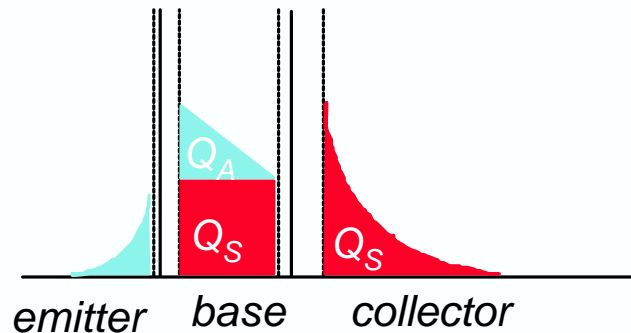


In saturation, there is additional minority carrier charge stored. Q_A represents the “active” part of the minority carrier charge; Q_S is the “saturation” charge.

$$Q_A = I_C t_F$$

$$Q_S = I_{BS} t_S \quad \text{where} \quad I_{BS} = I_B - I_C / \beta = \text{“base overdrive current”}$$

$$t_S = \frac{\alpha_F (t_F + \alpha_R t_R)}{1 - \alpha_F \alpha_R} = \text{“saturation time constant”}$$

RTL Propagation Delays: t_{PLH}

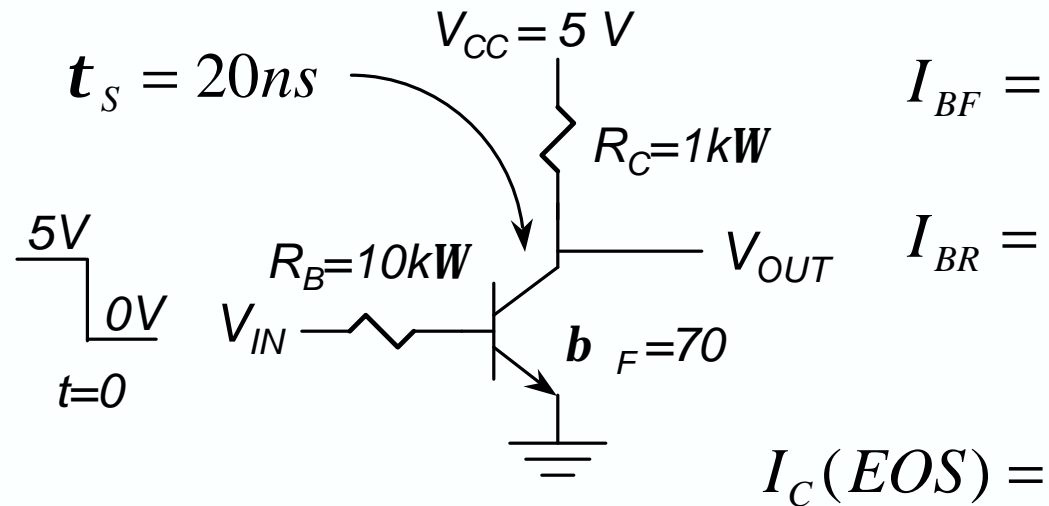


$$t_s =$$

$$t_r =$$


$$t_{PLH} =$$

Schottky Clamped Inverter

 

- The Schottky diode “turns on” at $V_{BC} = 0.3V$ so the transistor can not saturate.
- $V_{CE(min)} = 0.7V - 0.3V = 0.4V$
- t_f and t_r are increased slightly.
- There is no saturation delay.
- Schottky clamping drastically improves the switching speed of Schottky TTL gates.


RTL NAND Gate

 

If any input goes low, the associated transistor turns off and the output rises to V_{CC} .


Compared to the inverter, V_{OL} is degraded to $3V_{CES}$.

RTL NOR Gate

 

If any input goes high, the associated transistor turns on and the output goes low to V_{CES} .

Standard RTL (circa 1962)

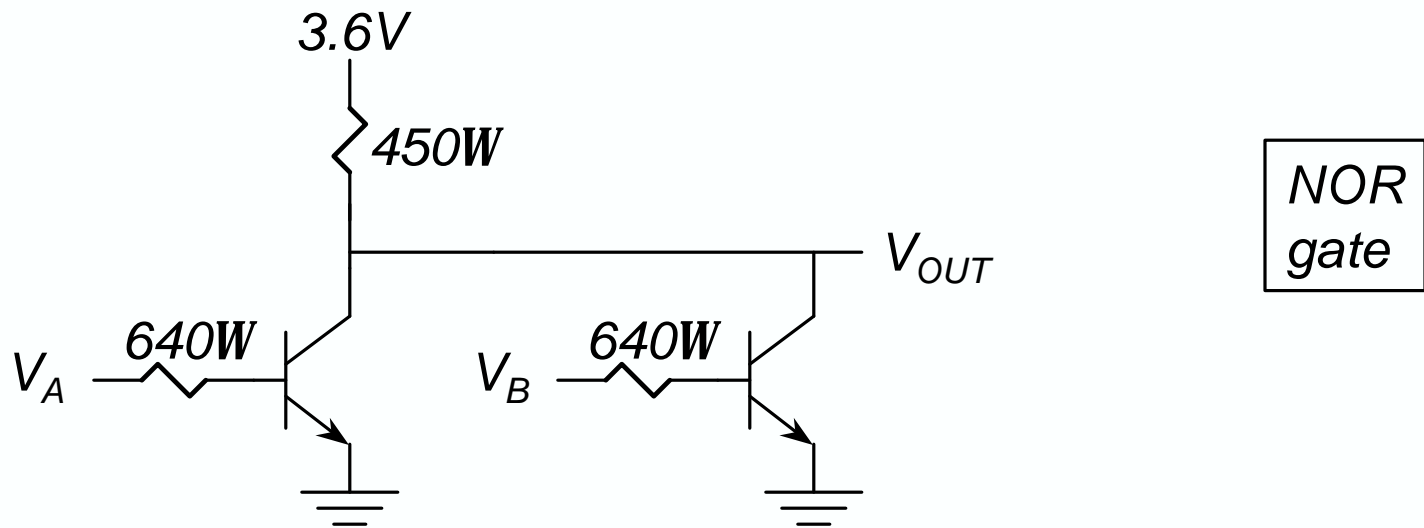

A decent PDP product was obtained ($16\text{mW} \times 12\text{ns} = 192\text{pJ}$), but at the expense of fanout ($N_{MAX} = 5$) as well as noise margins and logic swing (1V logic swing @ $N=5$).

By 1965, DTL replaced RTL.